

Single Stage Amplifiers

- ***Basic Concepts***
- ***Common Source Stage***
- ***Source Follower***
- ***Common Gate Stage***
- ***Cascode Stage***

Hassan Aboushady
University of Paris VI

References

- **B. Razavi, "Design of Analog CMOS Integrated Circuits", McGraw-Hill, 2001.**

Single Stage Amplifiers

- ***Basic Concepts***
- ***Common Source Stage***
- ***Source Follower***
- ***Common Gate Stage***
- ***Cascode Stage***

Hassan Aboushady
University of Paris VI

Basic Concepts I

- **Amplification is an essential function in most analog circuits !**
- **Why do we amplify a signal ?**
 - The signal is too small to drive a load
 - To overcome the noise of a subsequent stage
 - Amplification plays a critical role in feedback systems

In this lecture:

- Low frequency behavior of single stage CMOS amplifiers:
 - Common Source, Common Gate, Source Follower, ...
- Large and small signal analysis.
- We begin with a simple model and gradually add 2nd order effects

➡ **Understand basic building blocks for more complex systems.**


Approximation of a nonlinear system

Input-Output Characteristic of a nonlinear system

$$y(t) \approx \alpha_0 + \alpha_1 x(t) + \alpha_2 x^2(t) + \dots + \alpha_n x^n(t) \quad x_1 \leq x \leq x_2$$

In a sufficiently narrow range:
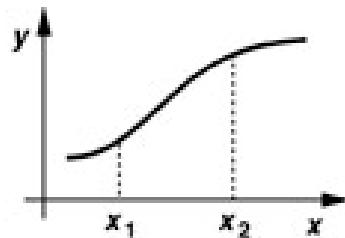
$$y(t) \approx \alpha_0 + \alpha_1 x(t)$$




where α_0 can be considered
the operating (bias) point and
 α_1 the small signal gain

H. Aboushady

University of Paris VI

Analog Design Octagon

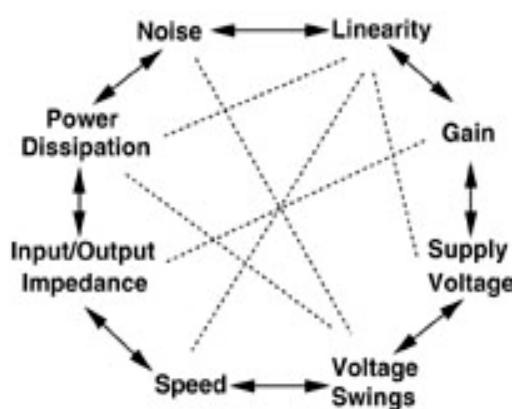

H. Aboushady


University of Paris VI

Single Stage Amplifiers


- **Basic Concepts**
- **Common Source Stage**
- **Source Follower**
- **Common Gate Stage**
- **Cascode Stage**

Hassan Aboushady
University of Paris VI

Common Source Stage with Resistive Load

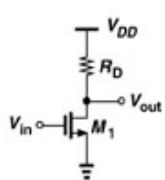

(a)

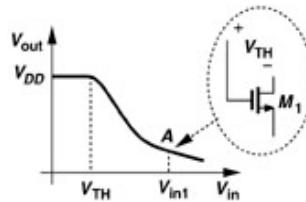

(b)

$$V_{out} = V_{DD} - R_D I_D$$


M1 in the saturation region: $V_{out} = V_{DD} - R_D \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{in} - V_{TH})^2$

M1 in limit of saturation: $V_{in1} - V_{TH} = V_{DD} - R_D \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{in1} - V_{TH})^2$


M1 in the linear region:

$$V_{out} = V_{DD} - R_D \mu_n C_{ox} \frac{W}{L} \left[(V_{in} - V_{TH}) V_{out} - \frac{V_{out}^2}{2} \right]$$


Common Source Stage with Resistive Load

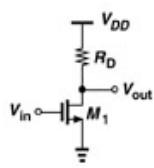

(a)

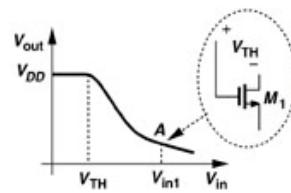

(b)

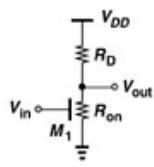

(c)

M1 in deep linear region:

$$V_{out} = V_{DD} \frac{R_{on}}{R_{on} + R_D} = \frac{V_{DD}}{1 + \mu_n C_{ox} \frac{W}{L} R_D (V_{in} - V_{TH})}$$



H. Aboushady

University of Paris VI

Common Source Stage with Resistive Load

M1 in the saturation region:

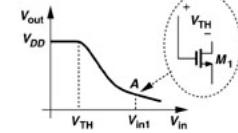
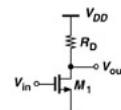
$$V_{out} = V_{DD} - R_D \frac{\mu_n C_{ox} W}{2 L} (V_{in} - V_{TH})^2$$



(b)

Small signal gain:
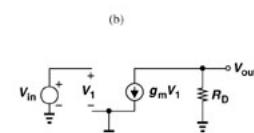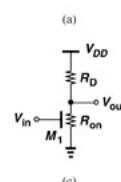
$$A_v = \frac{\partial V_{out}}{\partial V_{in}} = -R_D \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH}) \\ = -g_m R_D$$



Small signal model for the saturation region

Same relation can be derived from the small signal equivalent circuit




To minimize nonlinearity, the gain equation must be a weak function of signal dependent parameters such as g_m !

H. Aboushady

University of Paris VI

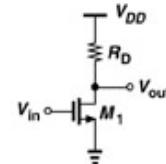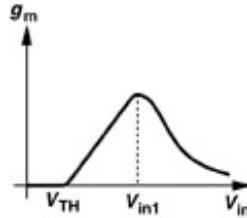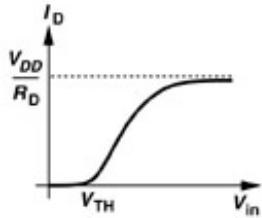Example 1

Sketch I_D and g_m of M1 as a function of the V_{in} :



• M1 in the saturation region:

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{in} - V_{TH})^2$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})$$

H. Aboushady

• M1 in the linear region:

$$I_D = \mu_n C_{ox} \frac{W}{L} \left[(V_{in} - V_{TH}) V_{out} - \frac{V_{out}^2}{2} \right]$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu_n C_{ox} \frac{W}{L} V_{out}$$

$$V_{out} = \frac{V_{DD}}{1 + \mu_n C_{ox} \frac{W}{L} R_D (V_{in} - V_{TH})}$$


University of Paris VI

Voltage Gain of a Common Source Stage

$$A_v = -g_m R_D$$

$$A_v = -\sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} \frac{V_{RD}}{I_D}$$
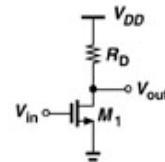
$$A_v = -\sqrt{2\mu_n C_{ox} \frac{W}{L}} \frac{V_{RD}}{\sqrt{I_D}}$$



How to increase A_v ?

Trade-offs:

- Increase W/L → Greater device capacitances.
- Increase V_{RD} → Limits V_{out} swing.
- Reduce I_D → Greater Time Constant.


H. Aboushady

University of Paris VI

Taking Channel Length Modulation into account

Calculating A_v starting from the Large Signal Equations:
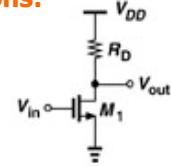
$$V_{out} = V_{DD} - R_D \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{in} - V_{TH})^2 (1 + \lambda V_{out})$$



$$A_v = \frac{\partial V_{out}}{\partial V_{in}} = -R_D \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH}) (1 + \lambda V_{out})$$

$$- R_D \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{in} - V_{TH})^2 \lambda \frac{\partial V_{out}}{\partial V_{in}}$$

$$A_v = -R_D g_m - R_D I_D \lambda A_v$$



$$A_v = -\frac{R_D g_m}{1 + R_D \lambda I_D} \xrightarrow{\lambda I_D = 1/r_o} A_v = -g_m \frac{r_o R_D}{r_o + R_D}$$

H. Aboushady

University of Paris VI

Taking Channel Length Modulation into account

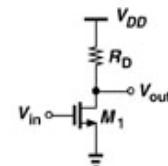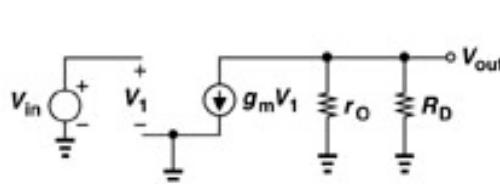Calculating A_v starting from the Small Signal model:



$$\left. \begin{aligned} g_m V_1 (r_o // R_D) &= -V_{out} \\ V_1 &= V_{in} \end{aligned} \right\} \quad A_v = \frac{V_{out}}{V_{in}} = -g_m (r_o // R_D)$$

H. Aboushady


University of Paris VI

Example 2

**Assuming M1 biased in saturation,
calculate the small signal voltage gain :**

- I_1 : Ideal current source \rightarrow Infinite Impedance

$$A_v = -g_m r_o$$

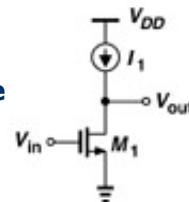

- **Intrinsic gain of a transistor:**

This quantity represents the maximum voltage gain that can be achieved using a single device.

$$I_{D1} = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{in} - V_{TH})^2 (1 + \lambda V_{out}) = I_1$$

- **Constant Current:**

As V_{in} increases, V_{out} must decrease such that the product remains constant


CS Stage with Current-Source Load

- Both transistors operate in the saturation region:

$$A_v = -g_m (r_{o1} // r_{o2})$$

- The output impedance and the minimum required VDS of M2 are less strongly coupled than the value and voltage drop of a resistor.

$$|V_{DS2,min}| = |V_{GS2} - V_{TH2}|$$

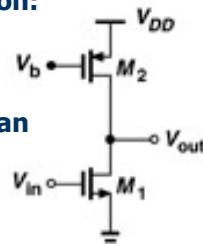

- This value can be reduced to a few hundred millivolts by simply increasing the width of M2.
- If r_{o2} is not sufficiently high, the length and width of M2 can be increased to achieve a smaller λ while maintaining the same overdrive voltage.
- The penalty is the large capacitance introduced by M2 at the output node.
- Increasing L2 while keeping W2 constant increases r_{o2} and hence the voltage gain, but at the cost of higher $|V_{DS2}|$ required to maintain M2 in saturation

CS with Source Degeneration

Large Signal model:

$$G_m = \frac{\partial I_D}{\partial V_{in}} = \frac{\partial I_D}{\partial V_{GS}} \frac{\partial V_{GS}}{\partial V_{in}}$$


$$V_{GS} = V_{in} - I_D R_S$$

$$\frac{\partial V_{GS}}{\partial V_{in}} = 1 - \frac{\partial I_D}{\partial V_{in}} R_S$$

$$G_m = \frac{\partial I_D}{\partial V_{GS}} \left(1 - R_S \frac{\partial I_D}{\partial V_{in}} \right)$$


$$G_m = g_m (1 - R_S G_m)$$

$$G_m = \frac{g_m}{1 + g_m R_S}$$

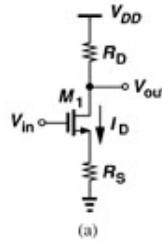

(a)

Small Signal model:

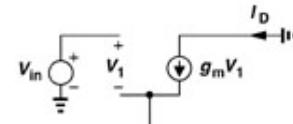

(b)

$$G_m = \frac{I_D}{V_{in}} = \frac{g_m V_1}{V_{in} + g_m V_1 R_S}$$

$$G_m = \frac{g_m}{1 + g_m R_S}$$

$$A_v = -G_m R_D$$

$$A_v = -\frac{g_m R_D}{1 + g_m R_S}$$

H. Aboushady

University of Paris VI

CS with Source Degeneration


$$G_m = \frac{g_m}{1 + g_m R_S} = \frac{1}{1/g_m + R_S} \quad \text{for } R_S \gg 1/g_m \Rightarrow G_m \approx 1/R_S$$

→ **I_D is linearized at the cost of lower gain.**

Small Signal model including body effect and channel length modulation:

$$I_{out} = g_m V_1 - g_{mb} V_X - \frac{V_X}{r_O}$$
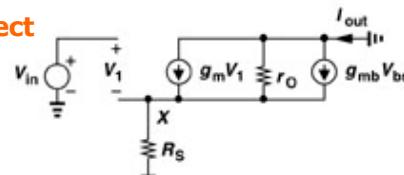
$$= g_m (V_{in} - I_{out} R_S) + g_{mb} (-I_{out} R_S) - \frac{I_{out} R_S}{r_O}$$






$$\Rightarrow G_m = \frac{I_{out}}{V_{in}} = \frac{g_m r_O}{R_S + [1 + (g_m + g_{mb}) R_S] r_O}$$

H. Aboushady

University of Paris VI

With and Without Source Degeneration
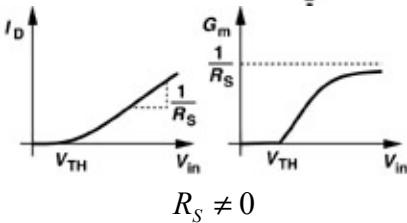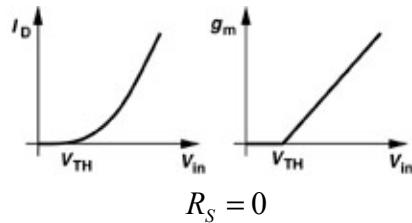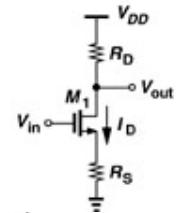
$$G_m = \frac{g_m r_o}{1 + [1 + (g_m + g_{mb}) R_s] r_o}$$




H. Aboushady

University of Paris VI

Estimating Gain by Inspection


$$A_v = -\frac{g_m R_D}{1 + g_m R_S} = -\frac{R_D}{1/g_m + R_S}$$
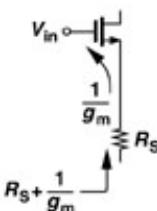
$$\text{Gain} = -\frac{\text{Resistance seen at the Drain}}{\text{Total Resistance in the Source Path}}$$




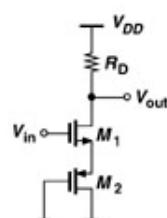Example:

$$A_v = -\frac{R_D}{1/g_{m1} + 1/g_{m2}}$$



(a)

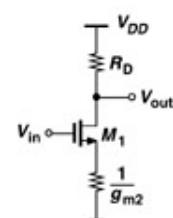

(b)

H. Aboushady


University of Paris VI

Output Resistance of Degenerated CS

$$V_1 = -I_X R_S$$

The current flowing in r_O :
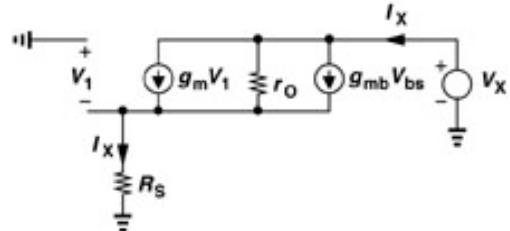
$$\begin{aligned} I_X - (g_m + g_{mb}) V_1 \\ = I_X + (g_m + g_{mb}) R_S I_X \end{aligned}$$



$$\Rightarrow V_X = r_O [I_X + (g_m + g_{mb}) R_S I_X] + I_X R_S$$

$$R_{out} = \frac{V_X}{I_X} = r_O [1 + (g_m + g_{mb}) R_S] + R_S$$

$$R_{out} = [1 + (g_m + g_{mb}) r_O] R_S + r_O$$

$$R_{out} \approx (g_m + g_{mb}) r_O R_S + r_O$$


$$\Rightarrow R_{out} = [1 + (g_m + g_{mb}) R_S] r_O$$

Voltage Gain of Degenerated CS

The current through R_S must equal that through R_D :

$$I_{R_D} = I_{R_S} = \frac{V_{out}}{R_D}$$
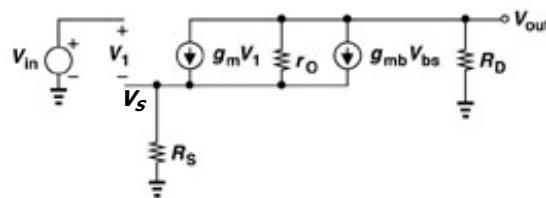
$$\Rightarrow V_S = -V_{out} \frac{R_S}{R_D}$$



$$\text{The current through } r_O : \quad I_{r_O} = -\frac{V_{out}}{R_D} - (g_m V_1 + g_{mb} V_{BS})$$

$$I_{r_O} = -\frac{V_{out}}{R_D} - [g_m (V_{in} + V_{out} \frac{R_S}{R_D}) + g_{mb} V_{out} \frac{R_S}{R_D}] \quad \Rightarrow \quad V_{out} = I_{r_O} r_O - \frac{V_{out}}{R_D} R_S$$

$$V_{out} = -\frac{V_{out}}{R_D} r_O - [g_m (V_{in} + V_{out} \frac{R_S}{R_D}) + g_{mb} V_{out} \frac{R_S}{R_D}] r_O - V_{out} \frac{R_S}{R_D}$$

$$\frac{V_{out}}{V_{in}} = -\frac{g_m r_O R_D}{R_D + R_S + r_O + (g_m + g_{mb}) R_S r_O}$$

Voltage Gain of Degenerated CS

$$\frac{V_{out}}{V_{in}} = -\frac{g_m r_o R_D}{R_D + R_S + r_o + (g_m + g_{mb}) R_S r_o}$$

$$\frac{V_{out}}{V_{in}} = -\frac{g_m r_o}{R_S + [1 + (g_m + g_{mb}) R_S] r_o} \frac{R_D [R_S + r_o + (g_m + g_{mb}) R_S r_o]}{R_D + R_S + r_o + (g_m + g_{mb}) R_S r_o}$$

$$\frac{V_{out}}{V_{in}} = G_m (R_{out} // R_D)$$

The output resistance of a degenerated CS stage:

$$R_{out} = [1 + (g_m + g_{mb}) R_S] r_o$$

The Transconductance of a degenerated CS stage:

$$G_m = \frac{I_{out}}{V_{in}} = \frac{g_m r_o}{R_S + [1 + (g_m + g_{mb}) R_S] r_o}$$


General expression to calculate A_v by inspection

Lemma:

$$Av = -G_m R_{out}$$

G_m : the transconductance of the circuit when the output is shorted to grounded.

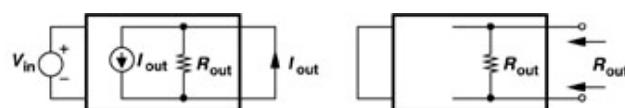R_{out} : the output resistance of the circuit when the input voltage is set to zero.



- For high voltage gain the output resistance must be high!
- A “buffer” is needed to drive a low-impedance load.
The source follower can operate as a voltage buffer.

Single Stage Amplifiers

- **Basic Concepts**
- **Common Source Stage**
- **Source Follower**
- **Common Gate Stage**
- **Cascode Stage**

Hassan Aboushady
University of Paris VI


Source Follower (Common Drain)

Large Signal Behavior

M1 turns on in saturation:

$$V_{out} = I_D R_S$$
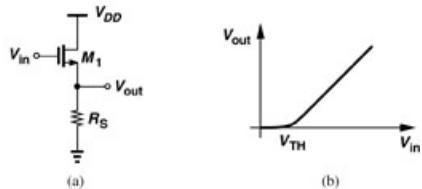
$$V_{out} = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{in} - V_{out} - V_{TH})^2 R_S$$



To calculate g_m:

$$\frac{\partial V_{out}}{\partial V_{in}} = \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{out} - V_{TH}) \left(1 - \frac{\partial V_{out}}{\partial V_{in}} - \frac{\partial V_{TH}}{\partial V_{in}} \right) R_S$$

$$\text{Since, } V_{TH} = V_{TH0} + \gamma \left(\sqrt{2\Phi_F + V_{SB}} - \sqrt{2\Phi_F} \right)$$

$$\begin{aligned} \frac{\partial V_{TH}}{\partial V_{in}} &= \frac{\partial V_{TH0}}{\partial V_{SB}} \frac{\partial V_{SB}}{\partial V_{in}} = \frac{\gamma}{2\sqrt{2\Phi_F + V_{SB}}} \frac{\partial V_{SB}}{\partial V_{in}} \\ &= \eta \frac{\partial V_{out}}{\partial V_{in}} \end{aligned}$$

Source Follower Voltage Gain

$$\frac{\partial V_{out}}{\partial V_{in}} = \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{out} - V_{TH}) \left(1 - \frac{\partial V_{out}}{\partial V_{in}} - \frac{\partial V_{TH}}{\partial V_{in}}\right) R_S$$

$$\frac{\partial V_{out}}{\partial V_{in}} = \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{out} - V_{TH}) \left(1 - \frac{\partial V_{out}}{\partial V_{in}} - \eta \frac{\partial V_{out}}{\partial V_{in}}\right) R_S$$

$$\frac{\partial V_{out}}{\partial V_{in}} = \frac{\mu_n C_{ox} \frac{W}{L} (V_{in} - V_{out} - V_{TH}) R_S}{1 + \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{out} - V_{TH}) R_S (1 + \eta)}$$

We also have, $g_m = \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{out} - V_{TH})$

$$Av = \frac{g_m R_S}{1 + (g_m + g_{mb}) R_S}$$


H. Aboushady

University of Paris VI

Source Follower Voltage Gain

Small Signal Equivalent Circuit
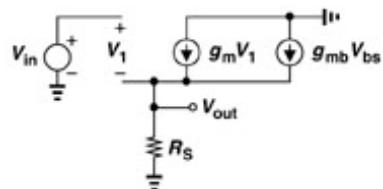
$$\begin{aligned} V_{out} &= [g_m V_1 + g_{mb} V_{BS}] R_S \\ &= [g_m (V_{in} - V_{out}) - g_{mb} V_{out}] R_S \end{aligned}$$




$$\Rightarrow Av = \frac{V_{out}}{V_{in}} = \frac{g_m R_S}{1 + (g_m + g_{mb}) R_S}$$

Since: $g_{mb} = \eta g_m$

And for: $g_m R_S \gg 1$
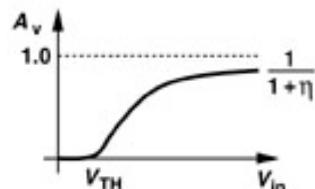
$$\Rightarrow Av \approx \frac{1}{(1 + \eta)}$$




H. Aboushady


University of Paris VI

Source Follower Output Resistance

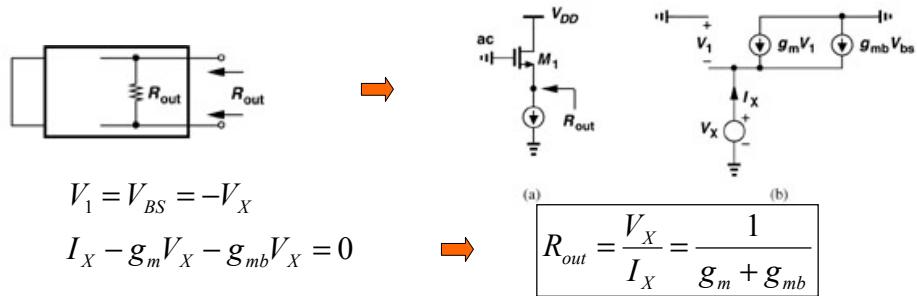R_{out} : the output resistance when the input voltage is set to zero.



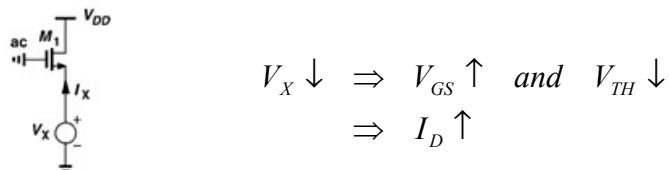Body Effect decreases the output resistance of source followers.




H. Aboushady

University of Paris VI

Source Follower body effect

R_{out} : the output resistance when the input voltage is set to zero.

Small Signal Model Simplification

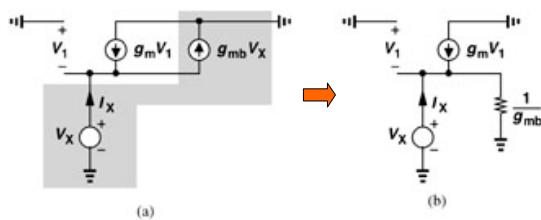


Note that the value of the current source $g_{mb} V_{bs}$ is linearly proportional to the voltage across it.

$$R_{out} = \frac{1}{g_m} // \frac{1}{g_{mb}} = \frac{1}{g_m + g_{mb}}$$

H. Aboushady

University of Paris VI

Source Follower Thévenin Equivalent

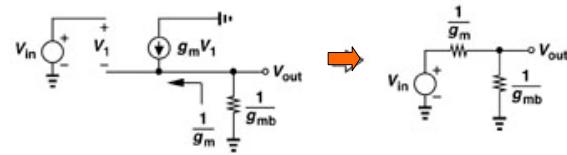


$$A_v = \frac{\frac{1}{g_{mb}}}{\frac{1}{g_m} + \frac{1}{g_{mb}}} = \frac{g_m}{g_m + g_{mb}}$$

H. Aboushady

University of Paris VI

Channel Length Modulation in M1 and M2

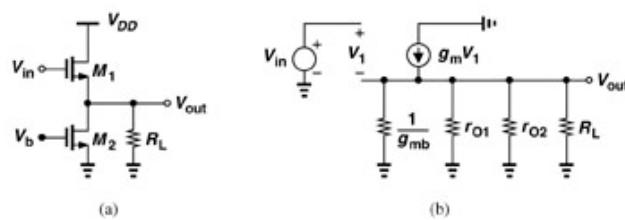

$$A_v = \frac{\frac{1}{g_{mb}} // r_{O1} // r_{O2} // R_L}{\frac{1}{g_{mb}} // r_{O1} // r_{O2} // R_L + \frac{1}{g_m}}$$

H. Aboushady

University of Paris VI


Source Follower Characteristics

+ High input impedance and Moderate output impedance

- Nonlinearity

$$V_{TH} \propto \sqrt{V_{SB}}$$

PMOS source follower with $V_{SB}=0$

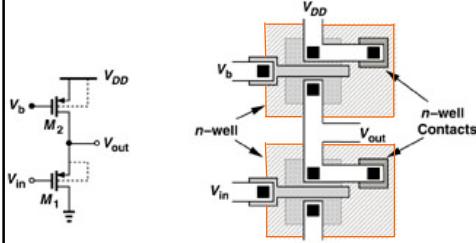


$$\begin{aligned} \mu_p < \mu_n &\Rightarrow g_{mp} < g_{mn} \\ &\Rightarrow R_{outp} > R_{outn} \end{aligned}$$

H. Aboushady

- Limited voltage swing

Example:

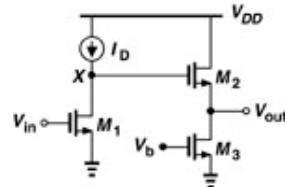

Without the source follower stage:

$$V_X > V_{GS1} - V_{TH1}$$


With the source follower stage:

$$V_X > V_{GS2} + (V_{GS3} - V_{TH3})$$

University of Paris VI


Low Load Impedance: CS vs SF

Source Follower Amplifier

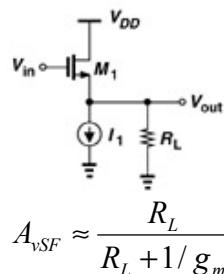

$$A_{vSF} \approx \frac{R_L}{R_L + 1/g_m}$$

Common Source Amplifier

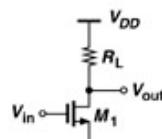

$$A_{vCS} \approx -g_m R_L$$

Assuming $R_L = 1/g_m$

$$A_{vSF} \approx 1/2$$

$$A_{vCS} \approx -1$$

→ Source Followers are not necessarily efficient drivers.

H. Aboushady

University of Paris VI

Single Stage Amplifiers

- **Basic Concepts**
- **Common Source Stage**
- **Source Follower**
- **Common Gate Stage**
- **Cascode Stage**

Hassan Aboushady
University of Paris VI

Common Gate Stage

Large Signal Behavior

$$V_{out} = V_{DD} - I_D R_D$$



Assuming M1 in saturation:

$$V_{out} = V_{DD} - \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_b - V_{in} - V_{TH})^2 R_D$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -\mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH}) \left(-1 - \frac{\partial V_{TH}}{\partial V_{in}} \right) R_D$$

$$\frac{\partial V_{out}}{\partial V_{in}} = \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH})(1 + \eta) R_D$$


$$\Rightarrow A_v = g_m (1 + \eta) R_D$$

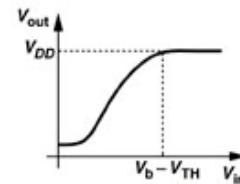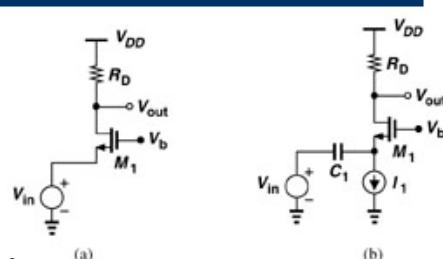

Common Gate Stage Input Resistance

Same as Output Resistance of Source Follower:

$$R_{in} = \frac{1}{g_m + g_{mb}}$$

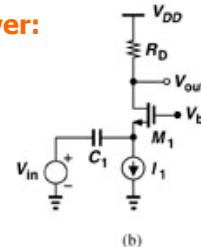


(b)

Body Effect:

- increases A_v
- decreases R_{in}

Common Gate Gain

Small Signal Signal Equivalent Circuit

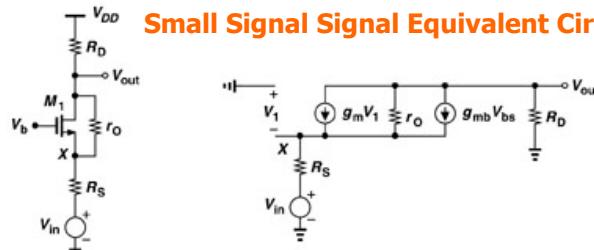

The current through R_s is equal to $-V_{out}/R_D$: $V_1 - \frac{V_{out}}{R_D} R_S + V_{in} = 0$

The current through r_o is equal to $-V_{out}/R_D - g_m V_1 - g_{mb} V_1$:

$$r_o \left(\frac{-V_{out}}{R_D} - g_m V_1 - g_{mb} V_1 \right) - \frac{V_{out}}{R_D} R_S + V_{in} = V_{out}$$

$$r_o \left[\frac{-V_{out}}{R_D} - (g_m + g_{mb}) \left(V_{out} \frac{R_S}{R_D} - V_{in} \right) \right] - \frac{V_{out}}{R_D} R_S + V_{in} = V_{out}$$

Common Gate Gain

Common Gate Amplifier:

$$A_{vCG} = \frac{(g_m + g_{mb})r_O + 1}{R_D + R_S + r_O + (g_m + g_{mb})r_O R_S} R_D$$

Degenerated Common Source Amplifier:

$$A_{vCS} = -\frac{g_m r_O}{R_D + R_S + r_O + (g_m + g_{mb})r_O R_S} R_D$$

Common Gate Stage Input Resistance

Since $V_I = -V_X$:



$$V_X = R_D I_X + r_O [I_X - (g_m + g_{mb})V_X]$$

$$\frac{V_X}{I_X} = \frac{R_D + r_O}{1 + (g_m + g_{mb})r_O}$$

$$R_{in} \approx \frac{R_D}{(g_m + g_{mb})r_O} + \frac{1}{(g_m + g_{mb})}$$


• Assume $R_D = 0$:
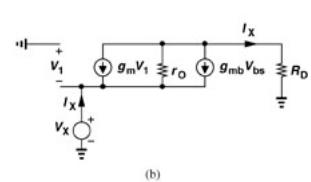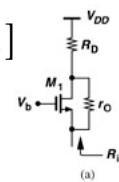
$$R_{in} = \frac{1}{1/r_O + (g_m + g_{mb})}$$



• Replace R_D by ideal current source:



$$R_{in} = \infty$$

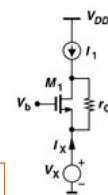

→ **R_{in} of a common gate stage is low only if R_D is small.**

Common Gate Stage Output Impedance

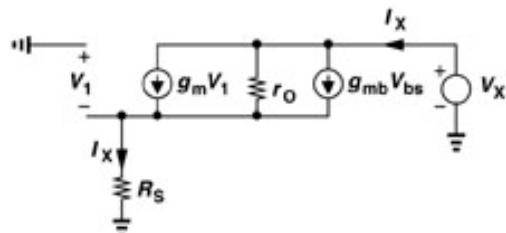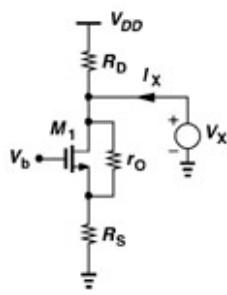Similar to Output Impedance of a Degenerated Common Source Stage



$$R_{out} = \left([1 + (g_m + g_{mb})r_o]R_s + r_o \right) // R_D$$

H. Aboushady

University of Paris VI

Single Stage Amplifiers

- **Basic Concepts**
- **Common Source Stage**
- **Source Follower**
- **Common Gate Stage**
- **Cascode Stage**

Hassan Aboushady
University of Paris VI

Biasing of a Cascode Stage

The cascade of CS stage and a CG stage is called "cascode".

- M1 : the input device
- M2 : the cascode device

Biasing conditions:

- M1 in saturation:

$$V_X = V_b - V_{GS2}$$



$$V_b - V_{GS2} \geq V_{in} - V_{TH1}$$

$$V_b \geq V_{in} + V_{GS2} - V_{TH1}$$

- M2 in saturation:

$$V_{out} - V_X \geq V_b - V_X - V_{TH2}$$
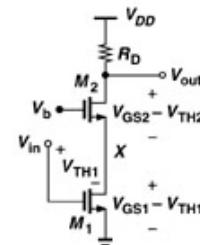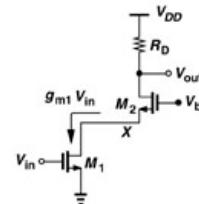
$$\boxed{V_{out} \geq V_{in} - V_{TH1} + V_{GS2} - V_{TH2}}$$




Cascode Stage Characteristics

Large signal behavior:

As V_{in} goes from zero to V_{DD}

For $V_{in} < V_{TH}$ M1 and M2 are OFF

$$\Rightarrow V_{out} = V_{DD}$$

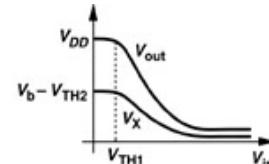


Output Resistance:

- Same common source stage with a degeneration resistor equal to r_{O1}


$$R_{out} = [1 + (g_{m2} + g_{mb2})r_{O2}]r_{O1} + r_{O2}$$
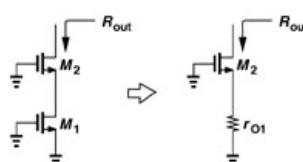
$$R_{out} \approx (g_{m2} + g_{mb2})r_{O2}r_{O1}$$



- M2 boosts the output impedance of M1 by a factor of $g_m r_{O2}$

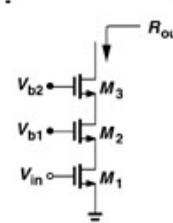- Triple cascode $R_{out} \uparrow\uparrow$
difficult biasing at low supply voltage.



Cascode Stage Voltage Gain


$$Av = -G_m R_{out}$$

$$G_m \approx g_{m1}$$

Ideal Current Source:

$$R_{out} \approx (g_{m2} + g_{mb2})r_{O2}r_{O1}$$

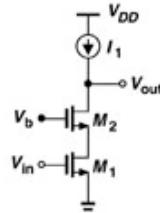
$$A_v \approx (g_{m2} + g_{mb2})r_{O2} g_{m1} r_{O1}$$



Cascode Current Source:

$$R_{out} \approx g_{m2}r_{O2}r_{O1} // g_{m3}r_{O3}r_{O4}$$
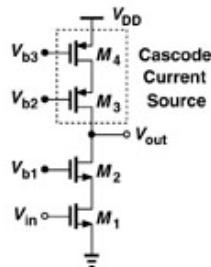
$$A_v \approx g_{m1}(g_{m2}r_{O2}r_{O1} // g_{m3}r_{O3}r_{O4})$$



H. Aboushady

University of Paris VI


Shielding Property

Assume V_x is higher than V_y by ΔV .


Calculate the resulting difference between I_{D1} and I_{D2} (with $\lambda \neq 0$).

$$I_{D1} - I_{D2} = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_b - V_{TH})^2 (\lambda V_{DS1} - \lambda V_{DS2})$$
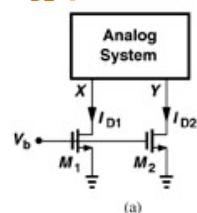
$$I_{D1} - I_{D2} = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_b - V_{TH})^2 (\lambda \Delta V_{DS})$$



(a)

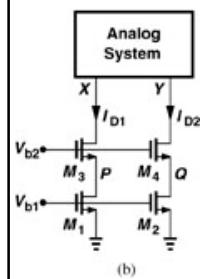

(b)


$$\Delta V_{PQ} = \Delta V \frac{r_{O1}}{[1 + (g_{m3} + g_{mb3})r_{O3}]r_{O1} + r_{O3}} \approx \frac{\Delta V}{(g_{m3} + g_{mb3})r_{O3}}$$

$$I_{D1} - I_{D2} = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_b - V_{TH})^2 \frac{\lambda \Delta V}{(g_{m3} + g_{mb3})r_{O3}}$$


H. Aboushady

University of Paris VI


Folded Cascode

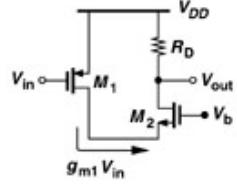

Simple Folded Cascode

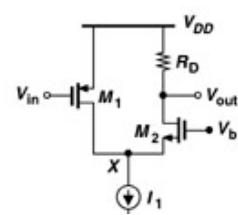


Folded Cascode with biasing

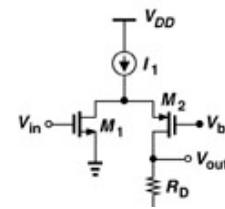


Folded Cascode with NMOS input

Large Signal Characteristics:

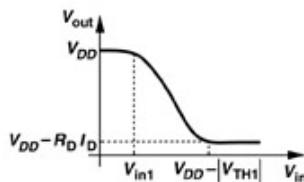

H. Aboushady

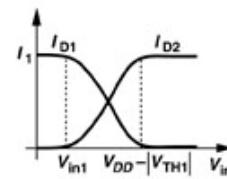


University of Paris VI

Output Resistance of Folded Cascode

Degenerated Common Source Stage:
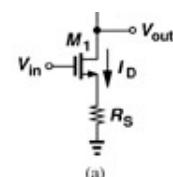
$$R_{out} = [1 + (g_{m1} + g_{mb1})r_{O1}]R_S + r_{O1}$$




(a)

Folded Cascode Stage:

$$M_1 \rightarrow M_2$$

$$R_S \rightarrow r_{o1} // r_{o3}$$
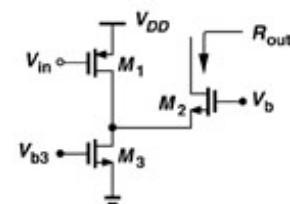
$$R_{out} = [1 + (g_{m2} + g_{mb2})r_{O2}](r_{O1} // r_{O3}) + r_{O2}$$



H. Aboushady

University of Paris VI