

Differential Amplifiers

- ***Single Ended and Differential Operation***
- ***Basic Differential Pair***
- ***Common-Mode Response***
- ***Differential Pair with MOS loads***

Hassan Aboushady
University of Paris VI

References

- **B. Razavi, "Design of Analog CMOS Integrated Circuits", McGraw-Hill, 2001.**

Differential Amplifiers

- **Single Ended and Differential Operation**
- **Basic Differential Pair**
- **Common-Mode Response**
- **Differential Pair with MOS loads**

Hassan Aboushady
University of Paris VI

Single Ended and Differential Operation


- **Single Ended Signal:**

- Measured with respect to a fixed potential, usually ground.

- **Differential Signal:**


- Measured between 2 nodes that have equal and opposite excursions around a fixed potential.

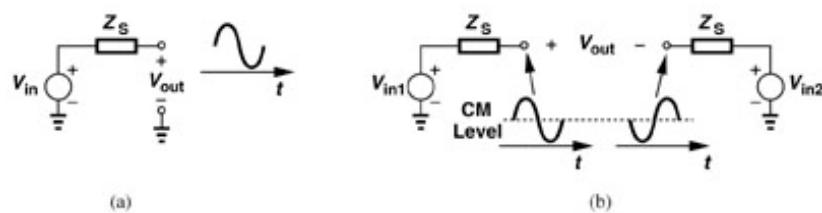- The center potential is called "Common Mode" (CM).




Rejection of Common Mode Noise

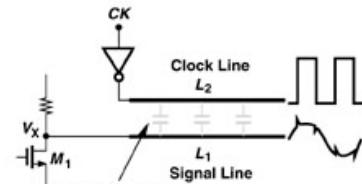- **Single Ended Signal:**
 - Due to capacitive coupling, transitions on the clock line corrupt the signal on L1 .



(a)

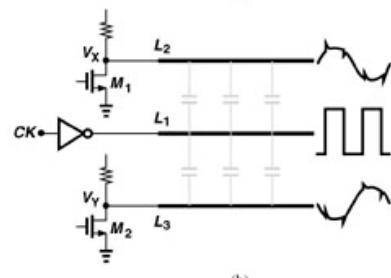- **Differential Signal:**
 - If the clock line is placed midway, the transitions disturb the differential signals by equal amounts, leaving the difference intact.




(b)


H. Aboushady

University of Paris VI

Rejection of Power Supply Noise

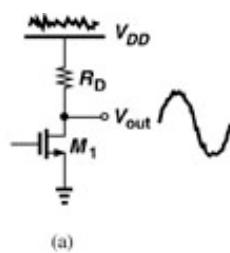

(a)

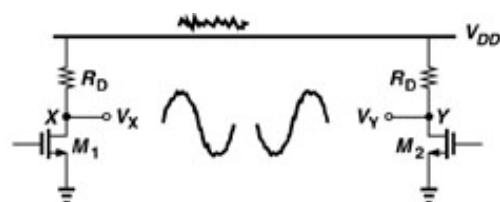

(b)

- **Maximum Output Swing:**

$$V_{out\max} = V_{DD} - (V_{GS} - V_{TH})$$

- **Maximum Output Swing:**

$$V_{X\max} - V_{Y\max} = 2[V_{DD} - (V_{GS} - V_{TH})]$$

H. Aboushady

University of Paris VI


Differential Pair

Differential circuit → sensitive to the input CM level.


$$\text{if } V_{in1} \neq V_{in2}$$

$$\Rightarrow I_{D1} \neq I_{D2}$$

$$\Rightarrow g_{m1} \neq g_{m2}$$

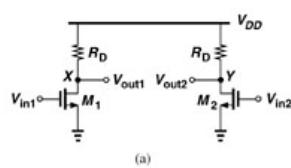

(a)

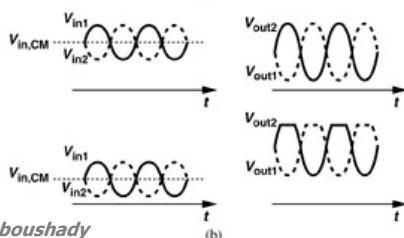

H. Aboushady

(b)


Differential pair → minimal dependence on input CM level.

$$I_{SS} = I_{D1} + I_{D2}$$

$$\text{if } V_{in1} = V_{in2}$$

$$\Rightarrow I_{D1} = I_{D2} = \frac{I_{SS}}{2}$$
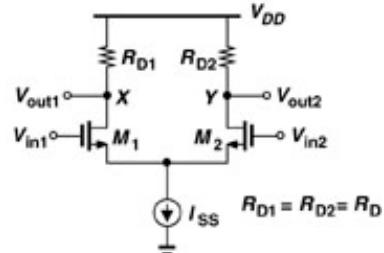
$$\text{Output CM} = V_{DD} - R_D \frac{I_{SS}}{2}$$



University of Paris VI

Differential Pair: Qualitative Analysis


$V_{in1} \ll V_{in2}$ → **M1 OFF, M2 ON**

$$I_{D2} = I_{SS} \rightarrow V_{out1} = V_{DD}$$

$$V_{out2} = V_{DD} - I_{SS} R_D$$

$V_{in1} = V_{in2}$ → **M1 ON, M2 ON**

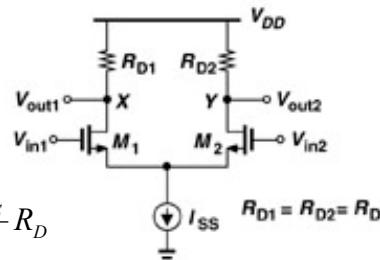
$$I_{D1} = I_{D2} = \frac{I_{SS}}{2} \rightarrow V_{out1} = V_{out2} = V_{DD} - \frac{I_{SS}}{2} R_D$$




$V_{in1} \gg V_{in2}$ → **M1 ON, M2 OFF**

$$I_{D1} = I_{SS} \rightarrow V_{out1} = V_{DD} - I_{SS} R_D$$

$$V_{out2} = V_{DD}$$

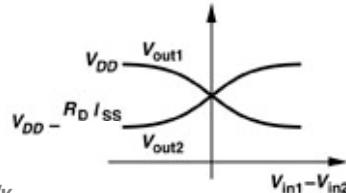


H. Aboushady

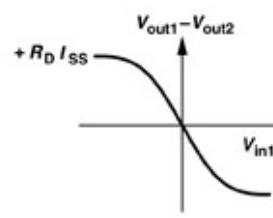

University of Paris VI

Differential Pair: Qualitative Analysis

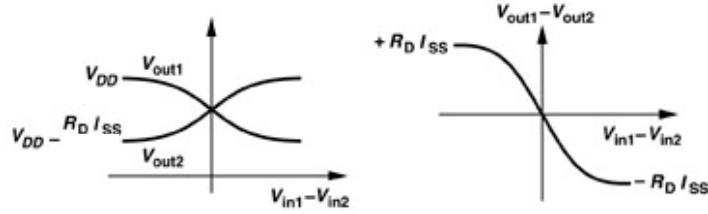

- Maximum and minimum levels are well-defined and independent of the input CM: V_{DD} and $V_{DD} - R_D I_{SS}$
- The small signal gain (the slope of $V_{out1}-V_{out2}$ vs $V_{in1}-V_{in2}$) is maximum for $V_{in1}=V_{in2}$ (equilibrium).

H. Aboushady

University of Paris VI

Differential Pair: Common-Mode Behavior

To study Common-Mode $\Rightarrow V_{in1} = V_{in2} = V_{in,CM}$






For proper operation:

• M3 in saturation

$$V_{in,CM} \geq V_{GS1} + (V_{GS3} - V_{TH3})$$

• M1 & M2 in saturation
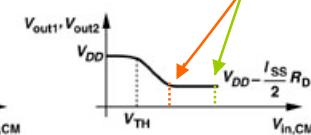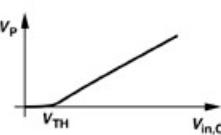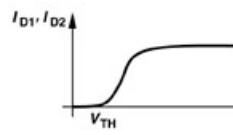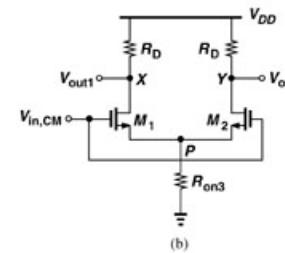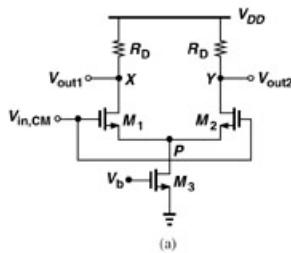
$$V_{in,CM} \leq V_{DD} - R_D \frac{I_{SS}}{2} + V_{TH}$$



H. Aboushady


University of Paris VI

Differential Pair: Output Voltage Swing

For M1 & M2 in saturation:

$$V_{out} - V_P \geq V_{in,CM} - V_P - V_{TH}$$

$$V_{out} \geq V_{in,CM} - V_{TH}$$

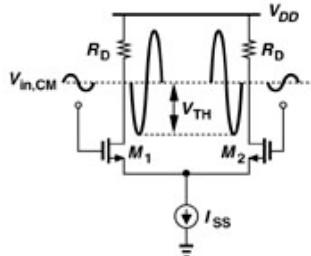

Output Voltage Swing:

$$V_{DD} \geq V_{out} \geq V_{in,CM} - V_{TH}$$

➡ To increase output swing, we choose a low $V_{in,CM}$

Differential Pair: Quantitative Analysis


$$V_P = V_{in1} - V_{GS1} = V_{in2} - V_{GS2}$$

$$[V_{in1} - V_{in2} = V_{GS1} - V_{GS2}] \quad (1)$$

Assuming M1 & M2 in saturation:

$$(V_{GS} - V_{TH})^2 = \frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}$$
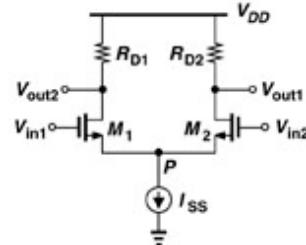
$$V_{GS} = \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} + V_{TH} \quad (2)$$



From eq. 1 & 2 :

$$V_{in1} - V_{in2} = \sqrt{\frac{2I_{D1}}{\mu_n C_{ox} \frac{W}{L}}} - \sqrt{\frac{2I_{D2}}{\mu_n C_{ox} \frac{W}{L}}}$$

Squaring the 2 sides, and since: $I_{SS} = I_{D1} + I_{D2}$

$$(V_{in1} - V_{in2})^2 = \frac{2}{\mu_n C_{ox} \frac{W}{L}} (I_{SS} - 2\sqrt{I_{D1}I_{D2}})$$


Differential Pair: Quantitative Analysis

Previous equation can be written:

$$\frac{\mu_n C_{ox} W}{2} \frac{V_{in1} - V_{in2}}{L} (V_{in1} - V_{in2})^2 - I_{SS} = -2\sqrt{I_{D1} I_{D2}}$$

Squaring the 2 sides, and since:
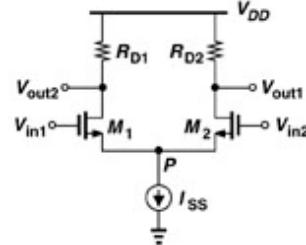
$$4I_{D1} I_{D2} = (I_{D1} + I_{D2})^2 - (I_{D1} - I_{D2})^2 \\ = I_{SS}^2 - (I_{D1} - I_{D2})^2$$



We arrive at:

$$(I_{D1} - I_{D2})^2 = -\frac{1}{4} \left(\mu_n C_{ox} \frac{W}{L} \right)^2 (V_{in1} - V_{in2})^4 + I_{SS} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2})^2$$

$$I_{D1} - I_{D2} = \frac{\mu_n C_{ox} W}{2} \frac{(V_{in1} - V_{in2})}{L} \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} W / L} - (V_{in1} - V_{in2})^2} \quad (3)$$

Differential Pair: Quantitative Analysis

Let $\Delta V_{in} = V_{in1} - V_{in2}$ and $\Delta I_D = I_{D1} - I_{D2}$

Deriving eq. 3 with respect to ΔV_{in}

$$G_m = \frac{\partial \Delta I_D}{\partial \Delta V_{in}} = \frac{\mu_n C_{ox} W}{2} \frac{\frac{4I_{SS}}{\mu_n C_{ox} W / L} - 2\Delta V_{in}^2}{\sqrt{\frac{4I_{SS}}{\mu_n C_{ox} W / L} - \Delta V_{in}^2}} \quad (4)$$

$$For \Delta V_{in} = 0, G_m = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}}$$

$$\text{Since: } V_{out1} - V_{out2} = V_{DD} - I_{D1} R_{D1} - V_{DD} - I_{D2} R_{D2}$$

$$\Delta V_{out} = \Delta I_D R_D \quad \Rightarrow \quad \Delta V_{out} = G_m \Delta V_{in} R_D$$

The small signal differential voltage gain:



$$|A_v| = \frac{\Delta V_{out}}{\Delta V_{in}} = G_m R_D = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS} R_D}$$

Drain Currents and Overall Transconductance

$$\Delta V_{in1} \text{ is when } I_{D1} = I_{SS} \rightarrow \Delta V_{in1} = V_{GS1} - V_{TH1} \rightarrow \Delta V_{in1} = \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} \quad (3)$$

$$I_{D1} - I_{D2} = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{in1} - V_{in2}) \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{in1} - V_{in2})^2} \quad (3)$$
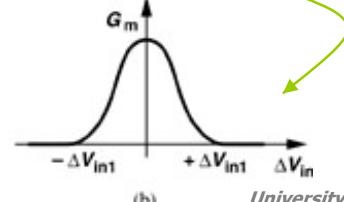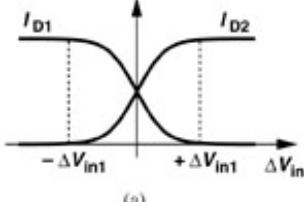
$$G_m = \frac{\mu_n C_{ox}}{2} \frac{W}{L} \frac{\frac{4I_{SS}}{\mu_n C_{ox} W / L} - 2\Delta V_{in}^2}{\sqrt{\frac{4I_{SS}}{\mu_n C_{ox} W / L} - \Delta V_{in}^2}} \quad (4)$$




H. Aboushady

University of Paris VI

ΔI_D vs ΔV_D

Plot the input-output characteristics of a differential pair as the device width and the tail current vary:
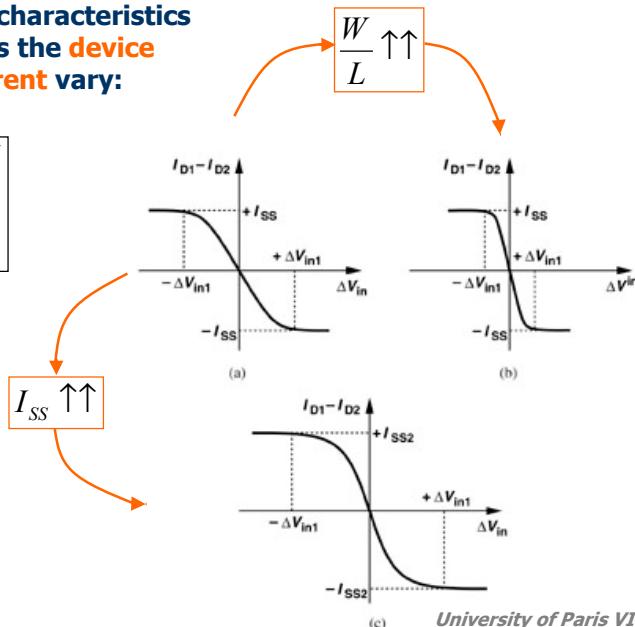
$$\Delta V_{in1} = \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$



H. Aboushady

University of Paris VI

Differential Pair: Small Signal Gain

$$|A_v| = \frac{\Delta V_{out}}{\Delta V_{in}} = G_m R_D = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS} R_D}$$

In equilibrium, we have

$$I_{D1} = I_{D2} = \frac{I_{SS}}{2}$$

$$A_v = g_m R_D$$

Where g_m is the transconductance of M1 & M2.

H. Aboushady

University of Paris VI

Calculating Small Signal Gain by Superposition

Set $V_{in2} = 0$

M1 forms a common source stage with a degeneration resistance


$$A_v = \frac{V_X}{V_{in1}} = -\frac{g_{m1} R_D}{1 + g_{m1} R_S}$$

Neglecting channel length modulation and body effect


$$R_S = 1/g_{m2}$$

$$\frac{V_X}{V_{in1}} = -\frac{g_{m1} R_D}{1 + g_{m1}/g_{m2}}$$

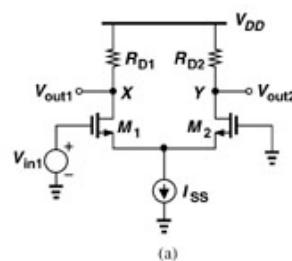
$$\rightarrow \frac{V_X}{V_{in1}} = -\frac{R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}} \quad (5)$$



(a)

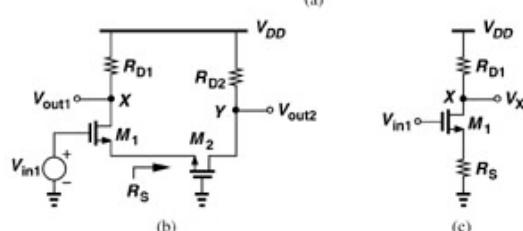

(b)

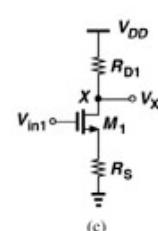


(c)

H. Aboushady

University of Paris VI

Calculating Small Signal Gain by Superposition

Replacing M1 by its Thévenin equivalent:

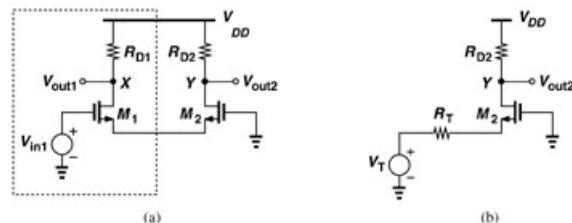

$$V_T = V_{in1} \quad R_T = 1/g_{m1} \quad R_{in2} = 1/g_{m2}$$

$$\rightarrow \boxed{\frac{V_Y}{V_{in1}} = \frac{R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}} \quad (6)$$

From eq. 5 & 6, we get:

$$(V_X - V_Y) \Big|_{due to V_{in1}} = \frac{-2R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}} V_{in1}$$

H. Aboushady

University of Paris VI

Calculating Small Signal Gain by Superposition

$$(V_X - V_Y) \Big|_{due to V_{in1}} = \frac{-2R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}} V_{in1}$$

Since: $g_{m1} = g_{m2} = g_m$

$$\rightarrow (V_X - V_Y) \Big|_{due to V_{in1}} = -g_m R_D V_{in1}$$

Similarly we can say that:

$$\rightarrow (V_X - V_Y) \Big|_{due to V_{in2}} = g_m R_D V_{in2}$$

The small signal differential voltage gain:


$$\boxed{\frac{(V_X - V_Y)_{total}}{V_{in1} - V_{in2}} = -g_m R_D}$$

H. Aboushady

University of Paris VI

The concept of Half Circuit

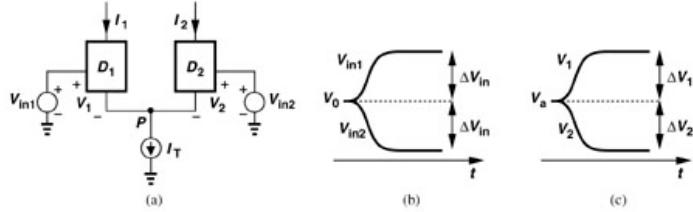
If a fully symmetric differential pair senses differential inputs then the concept of **half circuit** can be applied.



- A differential change in the inputs V_{in1} and V_{in2} is absorbed by V_1 and V_2 leaving V_P constant

Application of The Half Circuit Concept

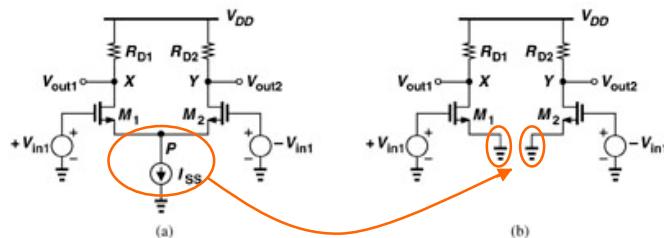Since V_P experiences no change, node P can be considered "ac ground" and the circuit can be decomposed into two separate halves




→ Two common source amplifiers:

$$\frac{V_X}{V_{in1}} = -g_m R_D \quad \frac{V_Y}{V_{in2}} = -g_m R_D$$

$$\boxed{\frac{V_X - V_Y}{V_{in1} - V_{in2}} = -g_m R_D}$$

The Half Circuit Concept : Example

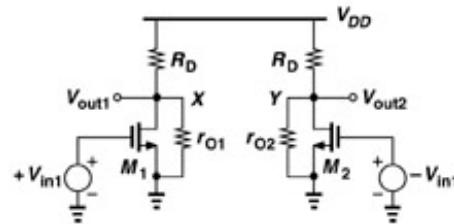Taking into account the output resistance
(channel length modulation)



→ Two common source amplifiers:

$$\frac{V_X}{V_{in1}} = -g_m(R_D // r_{O1}) \quad \frac{V_Y}{V_{in2}} = -g_m(R_D // r_{O2})$$


$$\boxed{\frac{V_X - V_Y}{V_{in1} - V_{in2}} = -g_m(R_D // r_O)}$$

H. Aboushady


University of Paris VI

Arbitrary Inputs to a Differential Pair

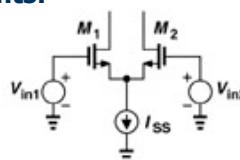
Conversion of arbitrary inputs to differential and common-mode components:



(a)

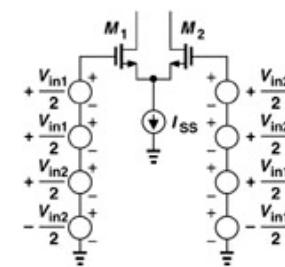


(b)

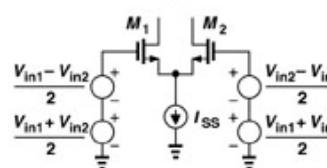

(c)

Common Mode

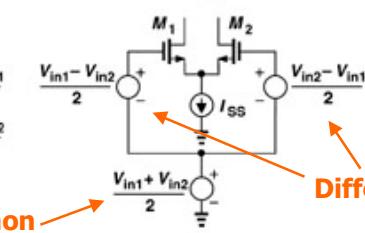

(d)


University of Paris VI

H. Aboushady

Differential

Arbitrary Inputs to a Differential Pair: Example

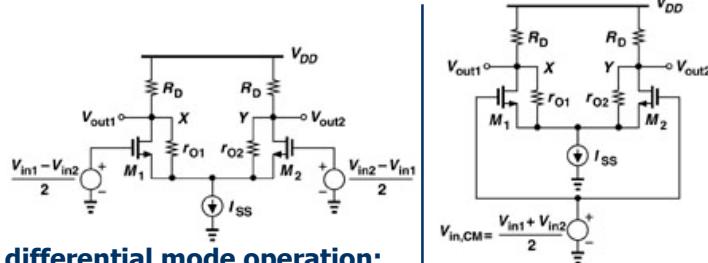Calculate V_X and V_Y if $V_{in1} \neq V_{in2}$ and $\lambda \neq 0$




For differential mode operation:

$$V_X = -g_m (R_D // r_{O1}) \frac{(V_{in1} - V_{in2})}{2}$$

$$V_Y = -g_m (R_D // r_{O2}) \frac{(V_{in2} - V_{in1})}{2}$$
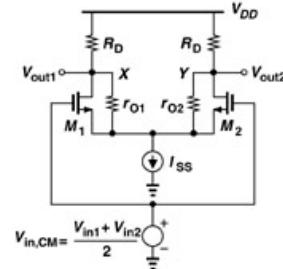
$$V_X - V_Y = -g_m (R_D // r_O) (V_{in1} - V_{in2})$$



For common mode operation:

$$I_{D1} = I_{D2} = I_{ss}/2$$

Assuming fully symmetric circuit and Ideal Current Source:

- I_{D1} and I_{D2} independent of $V_{CM,in}$
- V_X and V_Y independent of $V_{CM,in}$

The Differential pair circuit:

Amplifies $V_{in1} - V_{in2}$, Eliminates the effect of $V_{CM,in}$

H. Aboushady




University of Paris VI

Common Mode Response: Non-Ideal Current Source

Assuming fully symmetric circuit with finite output impedance current source, R_{SS} :

Equivalent circuit:
• Degenerated Common Source
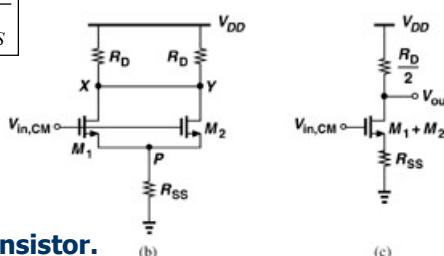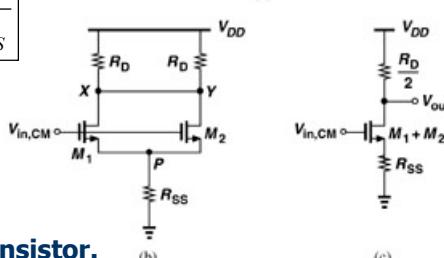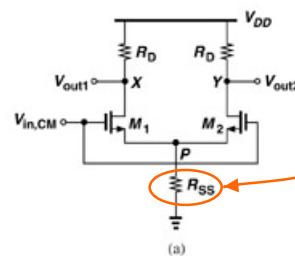
$$A_{v,CM} = \frac{V_{out}}{V_{in,CM}} = -\frac{R_D/2}{1/(2g_m) + R_{SS}}$$



g_m the transconductance of 1 transistor.

H. Aboushady


University of Paris VI

Common Mode Response: R_D Mismatch Effect

Assuming M1 & M2 identical:


$$\Delta V_X = -\Delta V_{in,CM} \frac{R_D}{1/(2g_m) + R_{SS}}$$
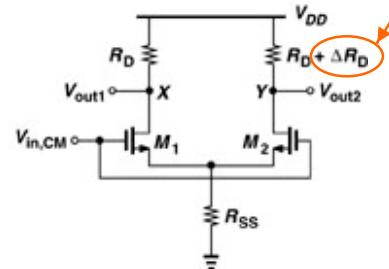
$$\Delta V_Y = -\Delta V_{in,CM} \frac{R_D + \Delta R_D}{1/(2g_m) + R_{SS}}$$



Common mode to differential conversion

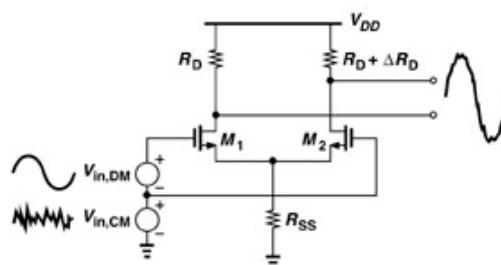Effect of CM noise in the presence of resistor noise



H. Aboushady

University of Paris VI

Common Mode Response: M_1-M_2 Mismatch Effect

$$I_{D1} = g_{m1}(V_{in,CM} - V_P)$$

$$I_{D2} = g_{m2}(V_{in,CM} - V_P)$$

$$V_P = (g_{m2} + g_{m1})(V_{in,CM} - V_P)R_{SS}$$


$$V_P = \frac{(g_{m2} + g_{m1})R_{SS}}{(g_{m2} + g_{m1})R_{SS} + 1} V_{in,CM}$$

$$V_X = -g_{m1}(V_{in,CM} - V_P)R_D \quad \Rightarrow \quad V_X = \frac{-g_{m1}}{(g_{m1} + g_{m2})R_{SS} + 1} R_D V_{in,CM}$$

$$V_Y = -g_{m2}(V_{in,CM} - V_P)R_D \quad \Rightarrow \quad V_Y = \frac{-g_{m2}}{(g_{m1} + g_{m2})R_{SS} + 1} R_D V_{in,CM}$$

$$V_X - V_Y = \frac{(g_{m1} - g_{m2})R_D V_{in,CM}}{(g_{m1} + g_{m2})R_{SS} + 1}$$
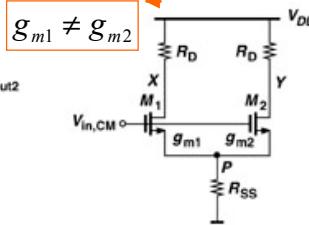
$$\text{CM to DM Conversion Gain: } \Rightarrow A_{CM-DM} = \frac{V_X - V_Y}{V_{in,CM}} = \frac{\Delta g_m R_D}{(g_{m1} + g_{m2})R_{SS} + 1}$$



Common Mode Rejection Ratio

$$CMRR = \left| \frac{A_{DM}}{A_{CM-DM}} \right|$$


A_{DM} : Differential Mode Gain

A_{CM-DM} : Common-Mode to Differential Mode Gain

H. Aboushady

University of Paris VI

Cascode Differential Pair

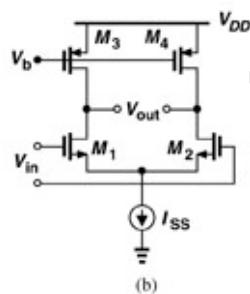



Current Source Load:

$$A_v = g_{mN} (r_{ON} // r_{OP})$$

Low gain 10 to 20.

To increase the gain:
Cascode Differential Pair
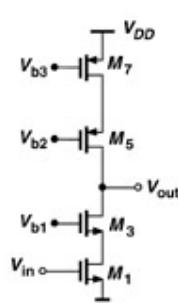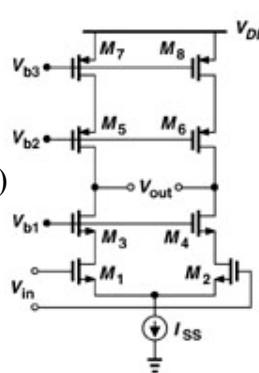
$$A_v = g_{m1} (g_{m3} r_{O3} r_{O1} // g_{m5} r_{O5} r_{O7})$$



H. Aboushady

University of Paris VI