

Frequency Response of Amplifiers

- ***General Considerations***
 - ***Miller Effect***
 - ***Association of Poles with Nodes***
- ***Common Source Stage***
- ***Source Follower***
- ***Differential Pair***


Hassan Aboushady
University of Paris VI

References

- **B. Razavi, "Design of Analog CMOS Integrated Circuits", McGraw-Hill, 2001.**

Miller Effect

- **Miller's Theorem**

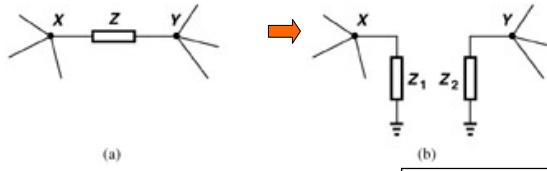

with $A_v = \frac{V_y}{V_x}$

we have

$$Z_1 = \frac{Z}{1 - A_v}$$

$$Z_2 = \frac{Z}{1 - A_v^{-1}}$$

- Proof

$$\frac{V_X - V_Y}{Z} = \frac{V_X}{Z_1} \quad \rightarrow \quad Z_1 = \frac{Z}{1 - \frac{V_Y}{V_X}}$$

$$\frac{V_Y - V_X}{Z} = \frac{V_Y}{Z_2} \quad \Rightarrow \quad Z_2 = \frac{Z}{1 - \frac{V_X}{V_Y}}$$

H. Aboushady


University of Paris VI

Example 1

- Calculate the input capacitance C_{in} :

$$Z_1 = \frac{1}{\frac{sC_F}{1+A}}$$

$$\rightarrow C_{in} = C_F(1 + A)$$

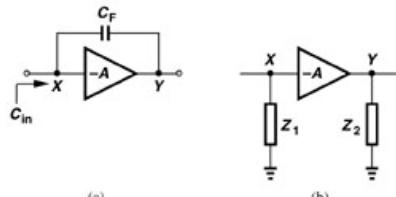

$A_v = \frac{V_y}{V_x}$ **should be calculated at the frequency of interest.**


To simplify calculations we usually use low frequency value of A_V .

Miller's theorem cannot be used simultaneously to calculate input-output transfer function and the output impedance.

H. Aboushady

University of Paris VI

Association of Poles with Nodes

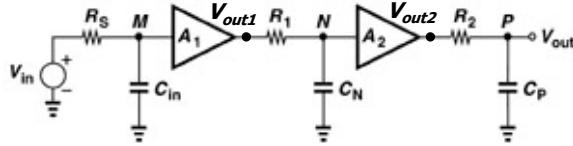

$$V_M(s) = \frac{V_{in}(s)}{R_S + \frac{1}{sC_{in}}} = \frac{V_{in}(s)}{1 + sR_SC_{in}}$$

$$V_N(s) = \frac{V_{out1}(s)}{1 + sR_1C_N}$$


$$V_P(s) = \frac{V_{out2}(s)}{1 + sR_2C_P}$$

$$\Rightarrow \frac{V_{out}}{V_{in}}(s) = \frac{A_1}{1 + sR_SC_{in}} \frac{A_2}{1 + sR_1C_N} \frac{1}{1 + sR_2C_P}$$

H. Aboushady

University of Paris VI

Association of Poles with Nodes

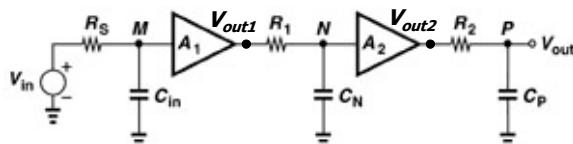

$$\frac{V_{out}}{V_{in}}(s) = \frac{A_1}{1 + sR_SC_{in}} \frac{A_2}{1 + sR_1C_N} \frac{1}{1 + sR_2C_P}$$

$$\omega_1 = \frac{1}{R_S C_{in}}$$

$$\omega_2 = \frac{1}{R_1 C_N}$$

$$\omega_3 = \frac{1}{R_2 C_P}$$

3 poles:

each determined by the total capacitance seen from each node to ground multiplied by the total resistance seen at the node to ground


H. Aboushady

University of Paris VI

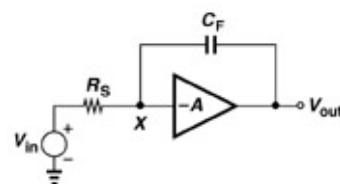Example 2

- Calculate the pole associated with node X:

The total equivalent capacitance seen from X to ground: $C_X = C_F(1 + A)$



The pole frequency:


$$\omega_X = \frac{1}{R_S C_X} = \frac{1}{R_S C_F(1 + A)}$$

Example 3

- Neglecting channel length modulation, compute the transfer function of the common gate stage with parasitic capacitances

Parasitic capacitances at node X: $C_S = C_{GS1} + C_{SB1}$

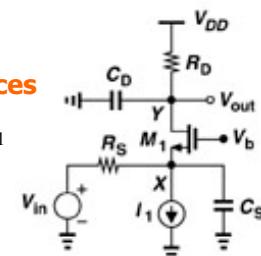Input resistance of a common gate amplifier: $R_{in} = \frac{1}{g_{m1} + g_{mb1}}$



Pole frequency at node X:

$$\omega_X = \frac{1}{(C_{GS1} + C_{SB1}) \left(R_S // \frac{1}{g_{m1} + g_{mb1}} \right)}$$

Parasitic capacitances at node Y: $C_D = C_{DG1} + C_{DB1}$


Pole frequency at node X:

$$\omega_Y = \frac{1}{(C_{DG1} + C_{DB1}) R_D}$$

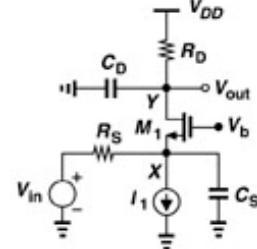Example 3 (cont.)

Low-frequency gain of a common gate stage neglecting channel length modulation:

$$A_{v0} = \frac{(g_m + g_{mb})R_D}{1 + (g_{m1} + g_{mb1})R_S}$$



The overall transfer function is given by:

$$\Rightarrow \frac{V_{out}(s)}{V_{in}(s)} = \frac{A_{v0}}{\left(1 + \frac{s}{\omega_{in}}\right) \left(1 + \frac{s}{\omega_{out}}\right)}$$

Note that if we do not neglect r_{o1} , the input and output nodes interact, making it difficult to calculate the poles.

Common Source Stage

Neglecting channel length modulation and applying the Miller's theorem on C_{GD} , we have:


The total capacitance at node X:

$$C_X = C_{GS} + (1 - A_v)C_{GD}$$

where, $A_v = -g_m R_D$

The 1st pole frequency:
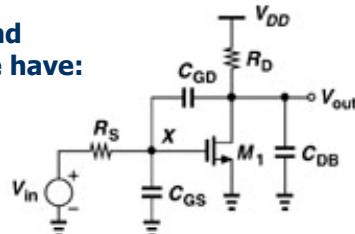
$$\omega_{p1} = \frac{1}{R_S(C_{GS} + (1 + g_m R_D)C_{GD})}$$



The total capacitance at the output node:

$$C_{out} = C_{DB} + (1 - A_v^{-1})C_{GD} \approx C_{DB} + C_{GD}$$


The 2nd pole frequency:

$$\omega_{p2} = \frac{1}{R_D(C_{DB} + C_{GD})}$$

Common Source Stage

The transfer function:
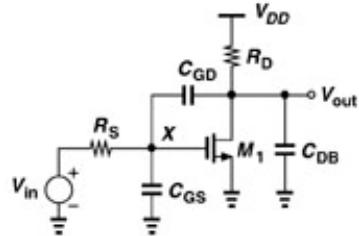
$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{-g_m R_D}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)}$$




r_0 and any load capacitance can be easily included.

Sources of error (approximation):

- we have not considered the existence of zeros in the circuit
- the amplifier gain varies with frequency

Common Source : "exact" Transfer Function

To obtain the exact transfer function:

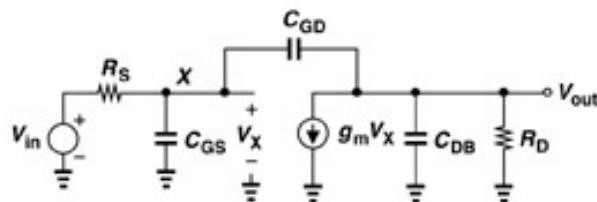

Applying Kirchoff Current Law (KCL):

$$\frac{V_X - V_{in}}{R_s} + sC_{GS}V_X + sC_{GD}(V_X - V_{out}) = 0$$

$$sC_{GD}(V_{out} - V_X) + g_m V_X + \left(sC_{DB} + \frac{1}{R_D}\right)V_{out} = 0$$

Common Source : "exact" 1st pole

After some manipulations, we get:

$$\frac{V_{out}}{V_{in}} = \frac{(sC_{GD} - g_m)R_D}{R_S R_D \xi s^2 + [R_S(1+g_m R_D)C_{GD} + R_S C_{GD} + R_S C_{GS} + R_D(C_{GD} + C_{DB})]s + 1}$$

with $\xi = C_{GS}C_{GD} + C_{GS}C_{DB} + C_{GD}C_{DB}$

Writing the denominator as: $D = \left(1 + \frac{s}{\omega_{p1}}\right)\left(1 + \frac{s}{\omega_{p2}}\right) = \frac{s^2}{\omega_{p1}\omega_{p2}} + \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}\right)s + 1$

Assuming $|\omega_{p1}| \ll |\omega_{p2}|$

$$\Rightarrow \omega_{p1} \approx \frac{1}{R_S(1+g_m R_D)C_{GD} + R_S C_{GD} + R_S C_{GS} + R_D(C_{GD} + C_{DB})}$$

Compare this result with ω_{in} calculated using Miller's Theorem

H. Aboushady

University of Paris VI

Common Source : "exact" 2nd pole

$$\frac{V_{out}}{V_{in}} = \frac{(sC_{GD} - g_m)R_D}{R_S R_D \xi s^2 + [R_S(1+g_m R_D)C_{GD} + R_S C_{GD} + R_S C_{GS} + R_D(C_{GD} + C_{DB})]s + 1}$$

with $\xi = C_{GS}C_{GD} + C_{GS}C_{DB} + C_{GD}C_{DB}$

having $D = \frac{s^2}{\omega_{p1}\omega_{p2}} + \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}\right)s + 1$

and $\omega_{p1} \approx \frac{1}{R_S(1+g_m R_D)C_{GD} + R_S C_{GD} + R_S C_{GS} + R_D(C_{GD} + C_{DB})}$

then $\omega_{p2} = \frac{1}{R_S R_D \xi} \frac{1}{\omega_{p1}}$

$$\Rightarrow \omega_{p2} = \frac{R_S(1+g_m R_D)C_{GD} + R_S C_{GS} + R_D(C_{GD} + C_{DB})}{R_S R_D(C_{GS}C_{GD} + C_{GS}C_{DB} + C_{GD}C_{DB})}$$

H. Aboushady

University of Paris VI

Comparison between "exact" and Miller's theorem

1st pole:

If

$$R_D(C_{GD} + C_{DB})$$

is negligible

exact

$$\omega_{p1} = \frac{1}{R_S(C_{GS} + (1 + g_m R_D)C_{GD}) + R_D(C_{GD} + C_{DB})}$$

Miller

$$\omega_{p1} = \frac{1}{R_S(C_{GS} + (1 + g_m R_D)C_{GD})}$$

2nd pole:

exact

$$\omega_{p2} = \frac{R_S(1 + g_m R_D)C_{GD} + R_S C_{GS} + R_D(C_{GD} + C_{DB})}{R_S R_D(C_{GS} C_{GD} + C_{GS} C_{DB} + C_{GD} C_{DB})}$$

$$\text{if } C_{GS} \gg (1 + g_m R_D)C_{GD} + \frac{R_D}{R_S}(C_{GD} + C_{DB})$$

$$\omega_{p2} \approx \frac{C_{GS}}{R_D(C_{GS} C_{GD} + C_{GS} C_{DB} + C_{GD} C_{DB})}$$

Miller

$$\omega_{p2} = \frac{1}{R_D(C_{DB} + C_{GD})}$$

H. Aboushady


University of Paris VI

Common Source : transfer function zero

After some manipulations, we get:

$$\frac{V_{out}}{V_{in}} = \frac{(sC_{GD} - g_m)R_D}{R_S R_D \xi s^2 + [R_S(1 + g_m R_D)C_{GD} + R_S C_{GD} + R_S C_{GS} + R_D(C_{GD} + C_{DB})]s + 1}$$

$$\omega_z = \frac{g_m}{C_{GD}}$$


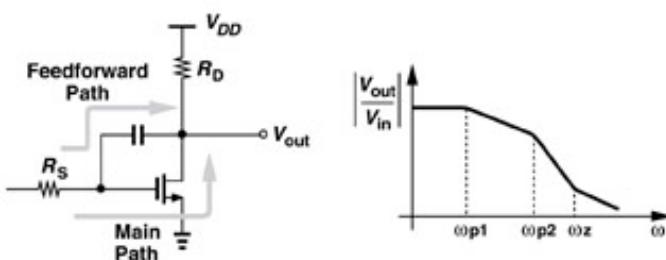


H. Aboushady

University of Paris VI

Source Follower

High frequency equivalent circuit

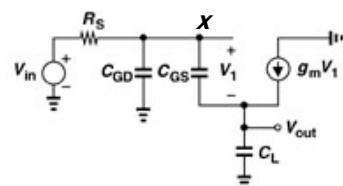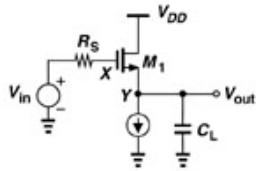

Applying Kirchoff Current Law (KCL)

at the output node: $sC_{GS}V_1 + g_m V_1 = sC_L V_{out}$

at node X: $\frac{V_{out} + V_1 - V_{in}}{R_S} + sC_{GD}(V_{out} + V_1) + sC_{GS}V_1 = 0$


$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{g_m + sC_{GS}}{R_S(C_{GS}C_L + C_{GS}C_{GD} + C_{GD}C_L)s^2 + (g_m R_S C_{GD} + C_L + C_{GS})s + g_m}$$

H. Aboushady

University of Paris VI

Source Follower Input Impedance
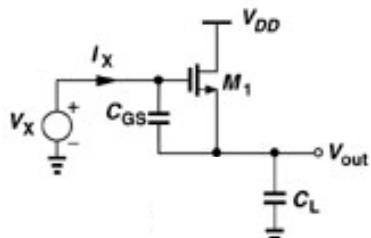
$$V_X = \frac{I_X}{sC_{GS}} + \left(I_X + \frac{g_m I_X}{sC_{GS}} \right) \frac{1}{sC_L}$$



Input Impedance:

$$\rightarrow Z_{in} = \frac{1}{sC_{GS}} + \frac{1}{sC_L} + \frac{g_m}{s^2 C_{GS} C_L}$$


Note the negative resistance: $\frac{-g_m}{\omega^2 C_{GS} C_L}$

H. Aboushady

University of Paris VI

Source Follower Output Impedance


Neglecting C_{GD}

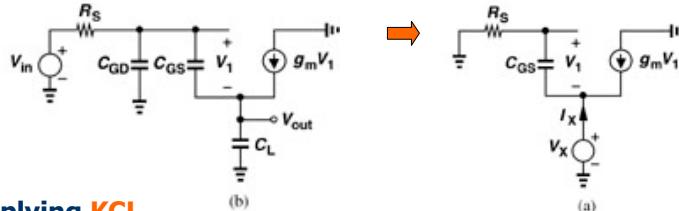

Applying KCL

$$sC_{GS}V_1 + g_mV_1 + I_X = 0$$
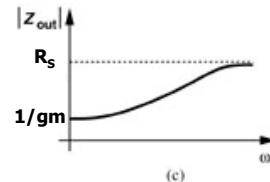
$$\frac{V_1}{R_S} + sC_{GS}(V_1 - V_X) = 0$$



Output Impedance:

$$Z_{out} = \frac{sC_{GS}R_S + 1}{sC_{GS} + g_m}$$



Z_{out} increases with frequency

It contains an inductive component

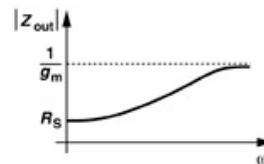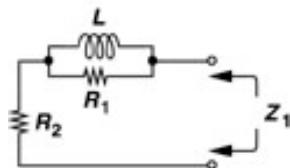H. Aboushady

University of Paris VI

Source Follower Output Impedance Equivalent C^t



Equivalent circuit of source follower output impedance:

$$at \quad \omega = \infty \Rightarrow Z_1 = R_1 + R_2$$

$$at \quad \omega = 0 \Rightarrow Z_1 = R_2$$

$$Z_1 = \frac{sLR_1}{sL + R_1} + R_2 \quad \Rightarrow \quad Z_1 = \frac{sL\left(\frac{1}{R_1} + \frac{1}{R_2}\right) + 1}{\frac{sL}{R_1R_2} + \frac{1}{R_2}} \quad \leftrightarrow \quad Z_{out} = \frac{sC_{GS}R_S + 1}{sC_{GS} + g_m}$$



$$R_1 = \left(R_S - \frac{1}{g_m} \right)$$


$$R_2 = \frac{1}{g_m}$$

$$L = \frac{C_{GS}}{g_m} \left(R_S - \frac{1}{g_m} \right)$$

H. Aboushady

University of Paris VI

Differential Pair

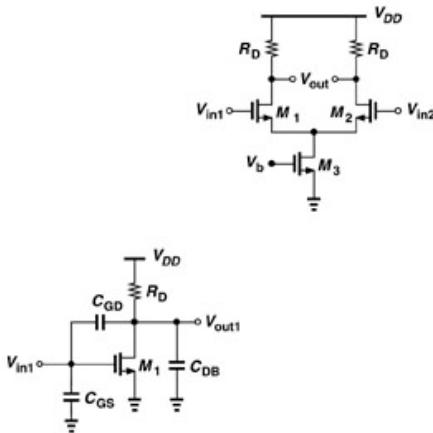


Differential inputs:
same as common source stage

H. Aboushady

University of Paris VI

Differential Pair

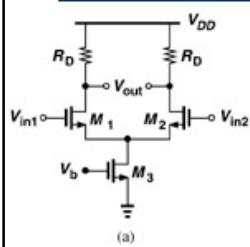


(a)

Common-Mode inputs:

Low frequency A_{CM} with M1-M2 mismatch:
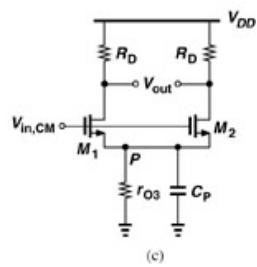
$$A_{CM} = \frac{\Delta g_m R_D}{(g_{m1} + g_{m2}) r_{o3} + 1}$$



(c)

High frequency A_{CM} with M1-M2 mismatch:

$$A_{CM} = \frac{\Delta g_m \left(R_D // \frac{1}{sC_L} \right)}{\left(g_{m1} + g_{m2} \right) \left(r_{o3} // \frac{1}{sC_P} \right) + 1}$$

where $C_P = C_{DG3} + C_{DB3} + C_{SB1} + C_{SB2}$

H. Aboushady

University of Paris VI